

NEC 304

STLD

Lecture 31

Read Only Memory (ROM)

Rajeev Pandey

Department Of ECE

rajeevvce2007@gmail.com

Overview


- Read-only memory can normally only be read
- Internal organization similar to SRAM
- ROMs are effective at implementing truth tables
 - Any logic function can be implemented using ROMs
- Multiple single-bit functions embedded in a single ROM
- Also used in computer systems for initialization
 - ROM doesn't lose storage value when power is removed
- Very useful for implementing FSMs

Read-Only Memory (ROM)

- **An array of semiconductor devices**
 - diodes
 - transistors
 - field effect transistors
- **2^N words by M bits**
- **Data can be read but not changed**
 - (normal operating conditions)


Read-Only Memory (ROM)

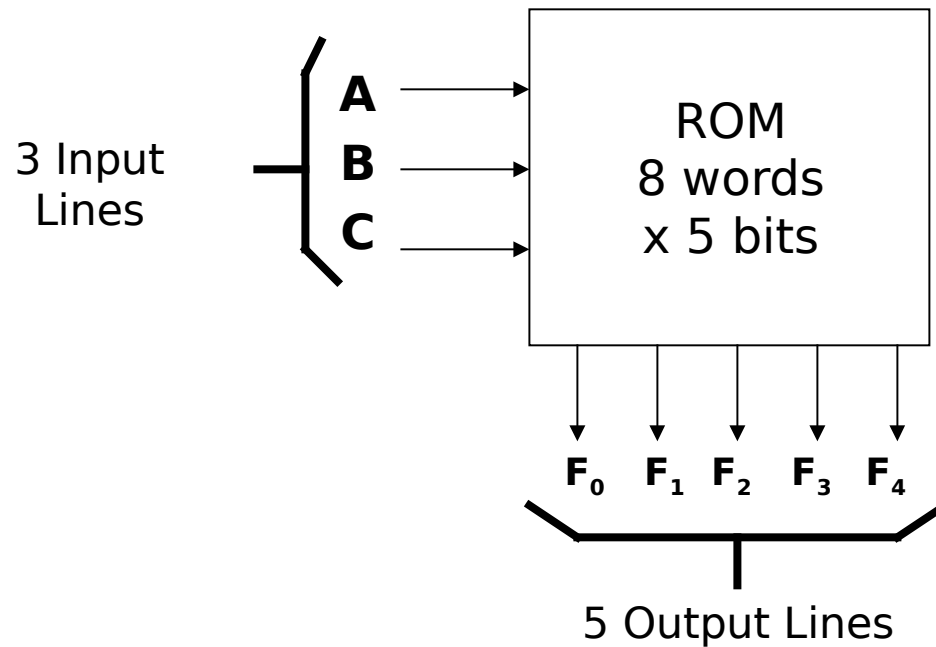- **N input bits**
- **2^N words by M bits**
- **Implement M arbitrary functions of N variables**
 - Example 8 words by 5 bits:



ROM Implementation

 - **ROM = "Read Only Memory"**
 - values of memory locations are fixed ahead of time
- **A ROM can be used to implement a truth table**
 - if the address is m -bits, we can address 2^m entries in the ROM.
 - our outputs are the bits of data that the address points to.



0	0	0	0	0	1	1
0	0	1	1	1	0	0
0	1	0	1	1	0	0
0	1	1	1	0	0	0
1	0	0	0	0	0	0
1	0	1	0	0	0	1
1	1	0	0	1	1	0
1	1	1	0	1	1	1

- m is the "height", and n is the "width"


ROM Implementation

- Suppose there are 10 inputs
10 address lines (i.e., $2^{10} = 1024$ different addresses)
- Suppose there are 20 outputs
- ROM is $2^{10} \times 20 = 20\text{K}$ bits (and a rather unusual size)
- Rather wasteful, since lots of storage bits
 - For functions, doesn't take advantage of K-maps, other minimization

Read-Only Memory (ROM)


Each minterm of each function can be specified

3 Inputs
Lines

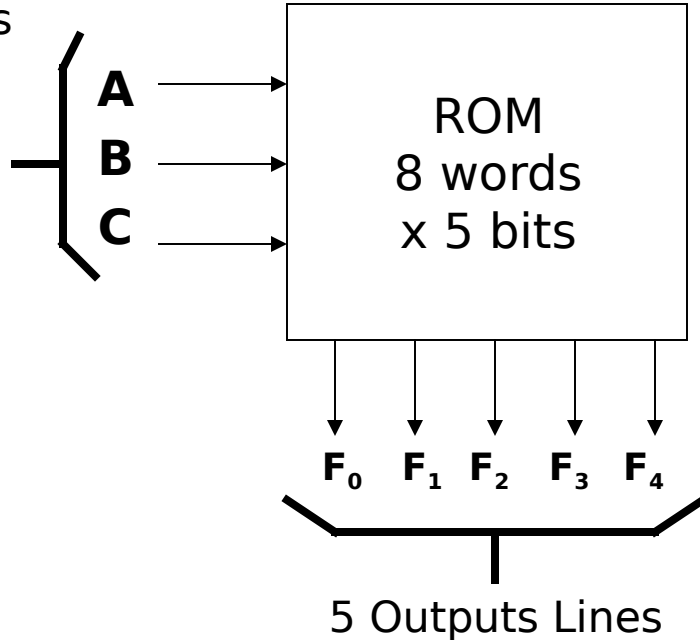


A	B	C	F ₀	F ₁	F ₂	F ₃	F ₄
0	0	0	0	1	0	1	0
0	0	1	1	1	1	1	0
0	1	0	0	0	0	1	1
0	1	1	1	1	1	0	1
1	0	0	0	1	0	1	0
1	0	1	0	1	1	1	1
1	1	0	1	0	1	0	1
1	1	1	1	1	0	1	0

ROM Internal Structure

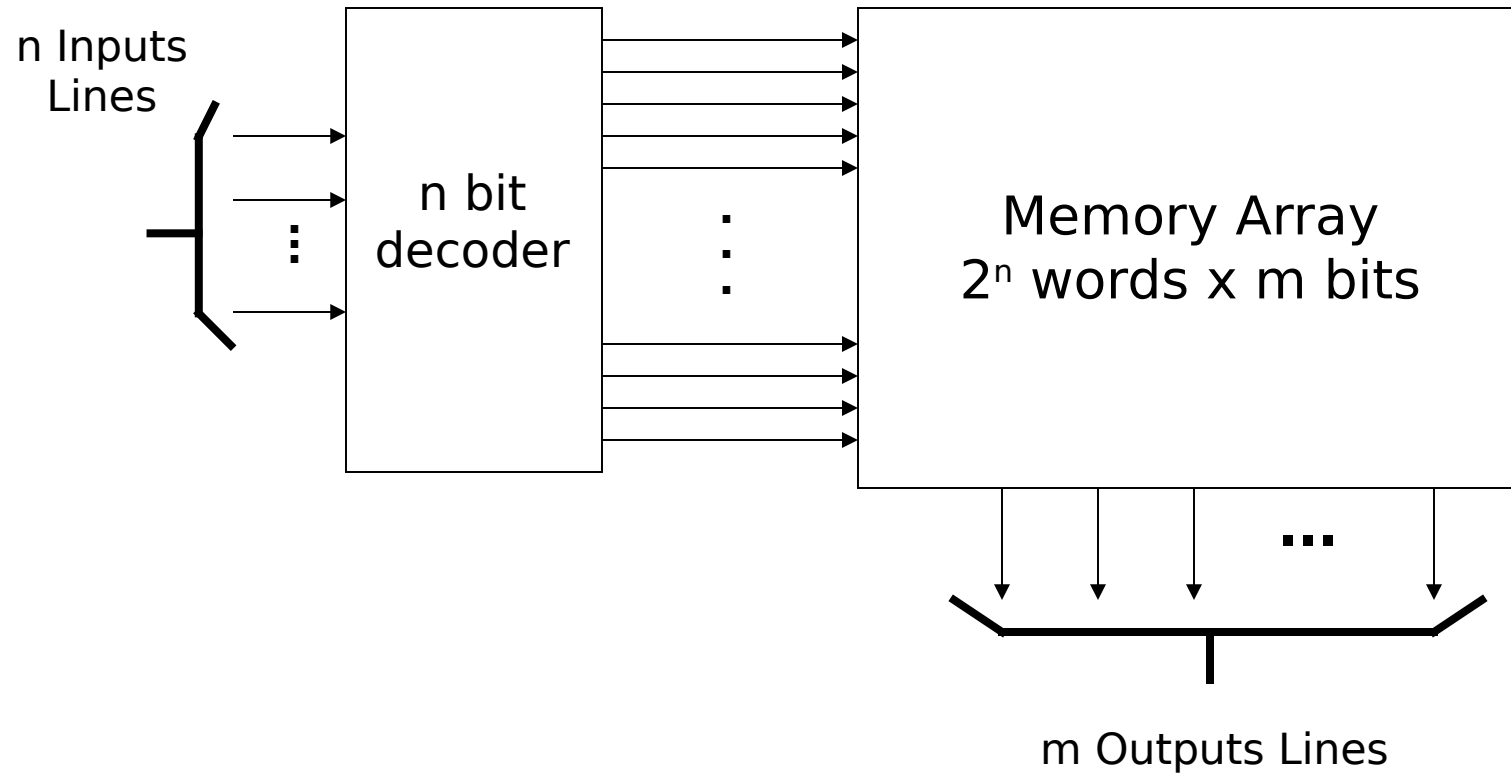

ROM Memory Array

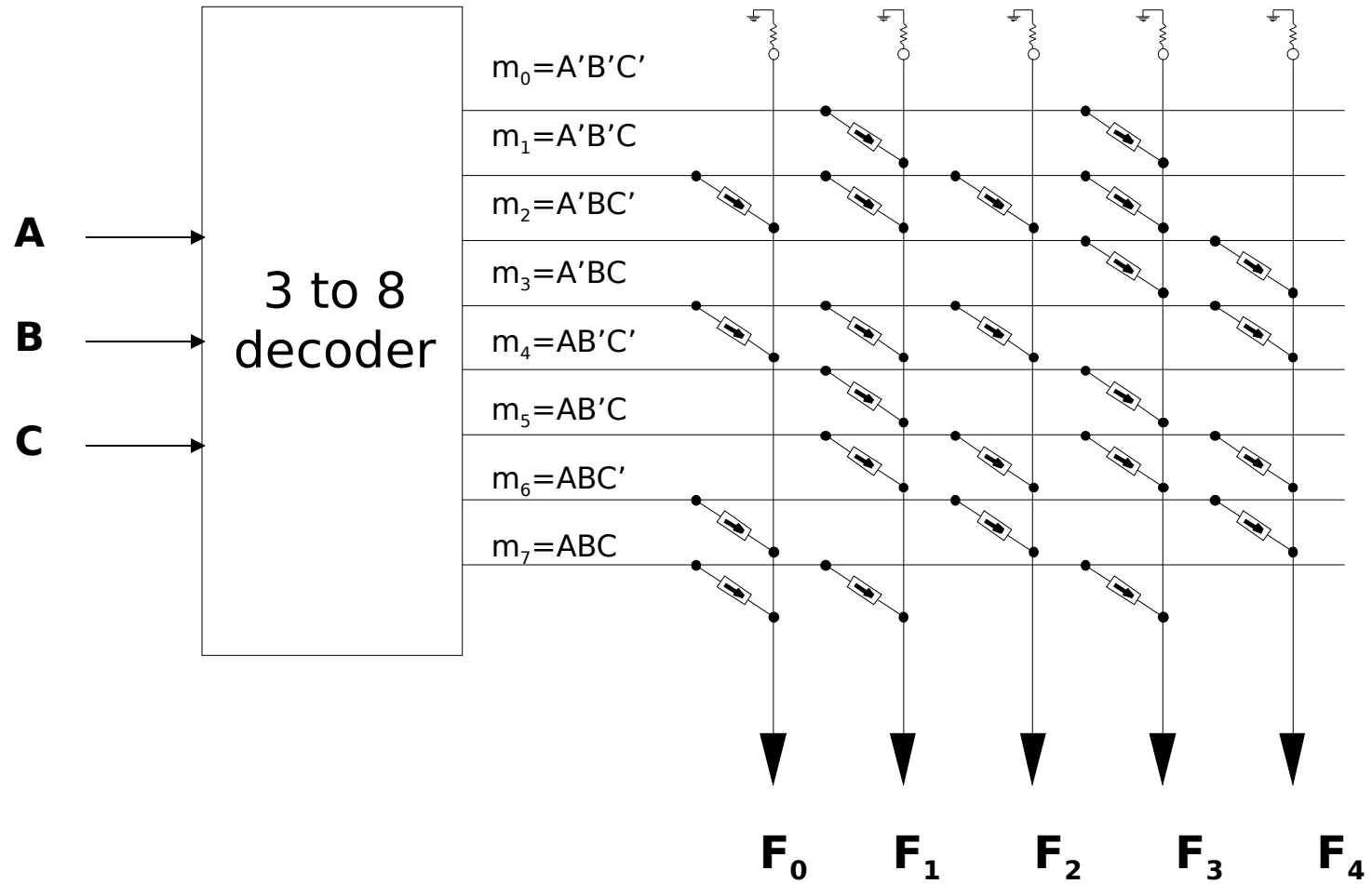

Inside the ROM

◦ Alternate view

- Each possible horizontal/vertical intersection indicates a possible connection

◦ Or gates at bottom output the word selected by the decoder (32×8)

 


Fig. 7-10 Internal Logic of a 32×8 ROM

ROM Example

Specify a truth table for a ROM which implements:

$$F = AB + A'BC'$$

$$G = A'B'C + C'$$

$$H = AB'C' + ABC' + A'B'C$$

A	B	C	F	G	H
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

ROM Example

Specify a truth table for a ROM which implements:

$$F = AB + A'BC'$$

$$G = A'B'C + C'$$

$$H = AB'C' + ABC' + A'B'C$$

A	B	C	F	G	H
0	0	0	0		
0	0	1	0		
0	1	0	1		
0	1	1	0		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		

ROM Example

Specify a truth table for a ROM which implements:


$$F = AB + A'BC'$$

$$G = A'B'C + C'$$

$$H = AB'C' + ABC' + A'B'C$$

A	B	C	F	G	H
0	0	0	0	1	0
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	0	0	0
1	0	0	0	1	1
1	0	1	0	0	0
1	1	0	1	1	1
1	1	1	1	0	0

Function Implementation

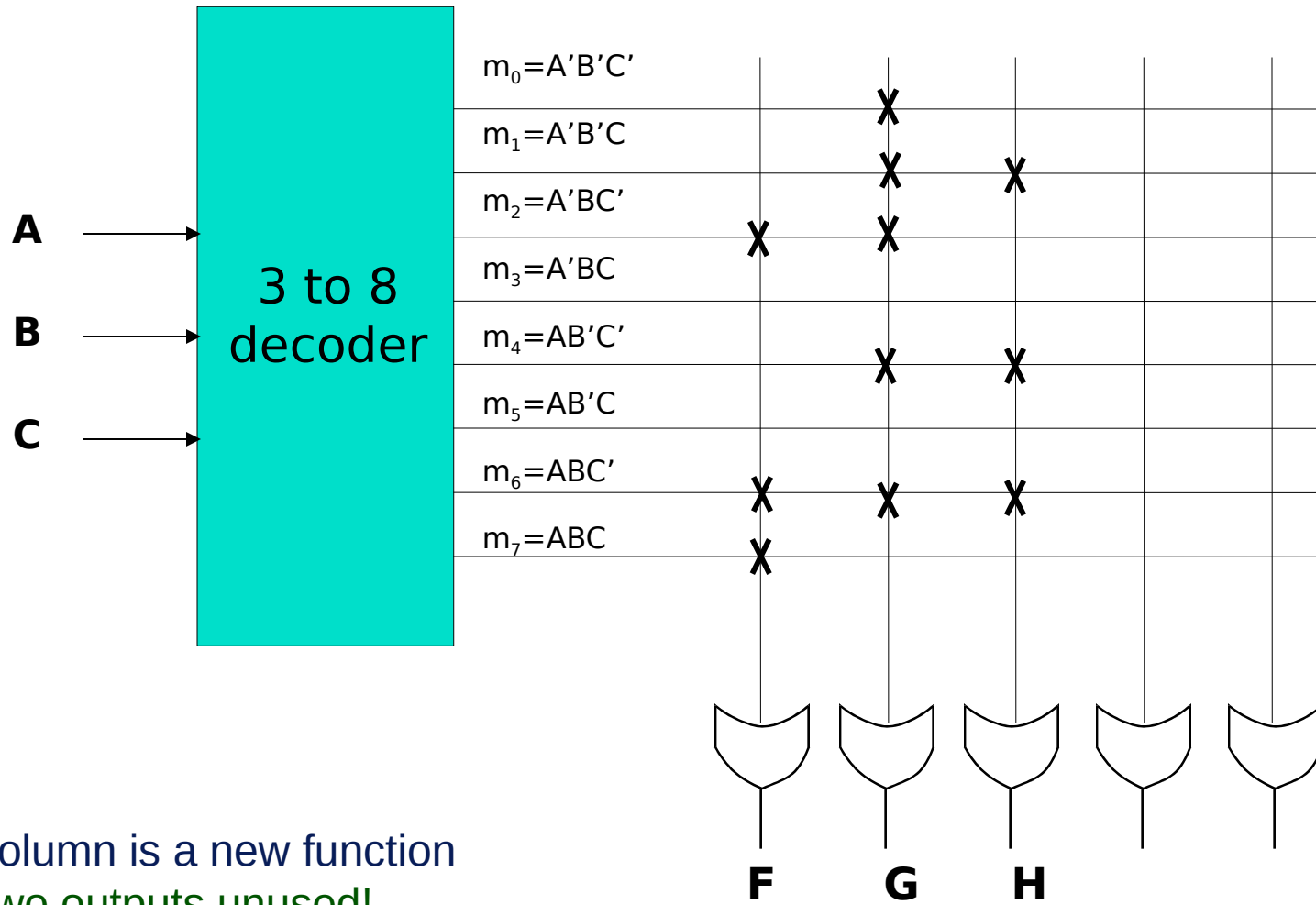


Each column is a new function

Note: two outputs unused!


ROM Implementation of a Moore Machine

 - ROMs implement combinational logic
- Note that ROMs **do not** hold state
- How would you determine the maximum clock frequency of this circuit?
 - Look at the FF to FF path (NS to PS)



ROM Implementation of a Mealy Machine

 - ROMs implement combinational logic
- Note that ROMs **do not** hold state
- How would you determine the maximum clock frequency of this circuit?
 - Look at the FF to FF path (NS to PS)



Summary

- ROMs provide stable storage for data
- ROMs have address inputs and data outputs
 - ROMs directly implement truth tables
- ROMs can be used effectively in Mealy and Moore machines to implement combinational logic
- In normal use ROMs are read-only
 - They are only read, not written
- ROMs are often used by computers to store critical information
 - Unlike SRAM, they maintain their storage after the power is turned off